
Fundamentals Of Microelectronics Solution Chapter 11

*Fundamentals
Of
Microelectronics
Solution
Chapter 11*

Downloaded from [turn-nyc-
edge-vdmdb.louper.io](https://turn-nyc-edge-vdmdb.louper.io) by
Carolyn & Ezra

For students and engineers delving into the world of analog integrated circuits, Behzad Razavi's *Fundamentals of Microelectronics* stands as a cornerstone textbook. Its rigorous yet accessible approach makes it a favorite in university courses worldwide. Among the most challenging and rewarding sections is Chapter 11, which typically addresses the frequency response of amplifiers.

Understanding this chapter is crucial because frequency response determines how an amplifier behaves across different signal frequencies—a key factor in modern high-speed and radio-frequency design. This article provides a comprehensive guide to mastering the **Fundamentals of Microelectronics Solution Chapter 11**, offering insights into core concepts, problem-solving strategies, and common pitfalls to

avoid.

WHAT DOES CHAPTER 11 COVER? A HIGH- LEVEL OVERVIEW

Before diving into solutions, it's essential to understand the chapter's scope. Chapter 11 in Razavi's *Fundamentals of Microelectronics* is dedicated to the frequency response of single-stage and multi-stage amplifiers. It builds upon the low-frequency small-signal models introduced earlier and extends them to include parasitic capacitances—both intrinsic (like C_{gs} , C_{gd} in MOSFETs) and extrinsic (like load and wiring capacitances). The goal is to analyze how gain, phase, and bandwidth are affected as the input signal

frequency varies.

Typical topics covered in this chapter include:

- Miller effect and its impact on input capacitance
- Poles and zeros in amplifier transfer functions
- Frequency response of common-source, common-gate, and common-drain stages
- High-frequency models of MOS and bipolar transistors
- Bandwidth estimation techniques (open-circuit time constants, short-circuit time constants)
- Cascode and differential pair frequency

behavior

When studying the **Fundamentals of Microelectronics Solution Chapter 11**, students often turn solution manuals to verify their work and clarify the step-by-step reasoning. A good solution not only provides the final answer but also explains the method—especially how to simplify complex circuits by identifying dominant poles.

**KEY CONCEPTS TO
MASTER BEFORE
ATTEMPTING
SOLUTIONS**

The Miller Effect: A

Quick Refresher

One of the most important concepts in Chapter 11 is the Miller effect. In an inverting amplifier, the capacitance between input and output (C_{gd} or C_{μ}) is multiplied by the voltage gain (plus one), effectively “appearing” larger at the input. This drastically reduces the amplifier’s bandwidth. Many problems in Chapter 11 ask you to compute the equivalent input capacitance due to Miller multiplication, so make sure you understand the derivation: $C_{in,eq} = C_{gd}(1 + A_v)$ for a common-source stage with gain A_v .

Poles and Zeros: The Language of Frequency Response

Every amplifier transfer function can be expressed as a ratio of polynomials in s (the complex frequency). The roots of the denominator polynomial are the poles; the roots of the numerator are the zeros. In the context of the **Fundamentals of Microelectronics**

Solution Chapter 11, you will spend considerable time determining these poles and zeros for various configurations. A single-stage common-source amplifier typically has two poles (one at input, one at output) and possibly a zero from feedforward through C_{gd} . Knowing how to approximate the dominant pole (the one at the lowest frequency) is key to estimating bandwidth without solving the full transfer function.

Open-Circuit and

Short- Circuit Time Constants

These methods are powerful for estimating bandwidth (or 3-dB frequency) in complex circuits. **Open-circuit time constant (OCT)** analysis assumes that when calculating the time constant for one capacitor, all other capacitors are replaced by open circuits (except for the capacitor under consideration). This gives an upper bound on the bandwidth. Conversely, **short-circuit time constants (SCTC)** are used for lower cutoff frequency in

capacitively coupled amplifiers. In many homework problems from Chapter 11, applying OCT correctly is often the hardest step—and solution guides clarify exactly which capacitors to short and which to open.

TYPICAL PROBLEM TYPES IN CHAPTER 11 SOLUTIONS

When you work through the **Fundamentals of Microelectronics Solution Chapter 11**, you will encounter several recurring problem families. Recognizing them early can save you time and reduce errors.

1. **Direct Calculation of Transfer Function:** Given a small-signal

model with explicit capacitances, derive V_{out}/V_{in} as a function of s . Usually involves nodal analysis and solving for the gain expression.

2. **Bandwidth Estimation without Full Transfer**

Function: Use OCT or SCTC to find the dominant time constant, then compute $f_{3dB} \approx 1/(2\pi\tau_{dom})$.

3. **Miller Effect Application:**

Find the equivalent input capacitance and then the new input pole frequency for a given amplifier circuit.

4. **Pole Splitting:**

In two-stage amplifiers (e.g., cascode), feedback through a compensation capacitor can split the poles, moving one to lower frequency and the other to higher frequency. Problems may ask you to calculate the new pole locations.

5. **Comparison of Topologies:**

Given multiple amplifier configurations (common-source, common-gate, etc.), rank them in terms of bandwidth and gain. This requires intuitive understanding of where poles

arise.

STEP-BY-STEP APPROACH TO SOLVING CHAPTER 11 PROBLEMS

Based on common solution strategies found in any reliable **Fundamentals of Microelectronics Solution Chapter 11** guide, here is a systematic method:

Step 1:
Draw the
High-
Frequency
Small-
Signal

Model

Replace each transistor with its high-frequency equivalent (including C_{gs} , C_{gd} , C_{db} for MOS; C_{π} , C_{μ} , C_{cs} for bipolar). Include any load or coupling capacitors explicitly. Label nodes clearly—input, output, and internal nodes.

Step 2:
Identify
the
Number
of
Independent

Capacitor actions

S

Each capacitor contributes one pole. However, capacitors connected between two nodes that are not grounded can be coupled. Use Miller transformation if the capacitor spans an inverting gain stage. For non-inverting stages, the analysis may be different.

In most exam and textbook problems, you are allowed to assume dominant pole behavior. Identify which capacitor likely creates the lowest frequency pole. Usually, the pole at the highest impedance node dominates. Use OCT to compute the time constant for each capacitor while shorting other capacitors (or opening them, depending on method).

Step 3:

Simplify

Using

Approxim

Step 4:

Write the

Transfer

Function (if required)

Apply nodal analysis. Write KCL at each node. Solve for V_{out}/V_{in} . A systematic approach: express node voltages in terms of V_{in} and V_{out} , then eliminate intermediate variables. The solution should yield a rational function: $H(s) = A_0 (1 + s/\omega_{z1}) \dots / (1 + s/\omega_{p1}) \dots$

Step 5: Compute Key Metrics

- **Midband Gain (A_0):** Gain at

frequencies where all capacitors are shorted (or open, depending on coupling).

- **3-dB Bandwidth (f_{-3dB}):** Frequency at which gain drops by 3 dB from midband.
- **Gain-Bandwidth Product (GBW):** For single-pole systems, $GBW = A_0 \times f_{-3dB}$.

COMMON PITFALLS AND HOW TO AVOID THEM

Even with a good solution manual, students often repeat the same mistakes. By learning from these errors, you can make your study of the **Fundamentals of Microelectronics**

Solution Chapter 11

more efficient.

- **Ignoring the Miller Effect:**

Forgetting to multiply the gate-drain capacitance by (gain+1) leads to underestimating input capacitance and overestimating bandwidth. Always check if the stage is inverting.

- **Confusing Open-Circuit vs. Short-Circuit Time Constants:**

OCT is used for upper cutoff (high-frequency roll-off) in direct-coupled amplifiers. SCTC is for lower cutoff in capacitively coupled stages. Using the wrong

method gives an incorrect 3-dB frequency.

- **Assuming All Poles are Real:**

In some circuits (e.g., cascodes with feedback), poles can become complex. Solutions often neglect this, but be aware that bandwidth estimates may be optimistic if overshoot occurs.

- **Neglecting Output Resistance:**

Transistors have finite output resistance (r_o), which affects both gain and pole locations. Many students treat r_o as infinite when it is not.

- **Unit Errors:**

Capacitances are often in femtofarads or picofarads, resistances in kilo-ohms. Always convert to base units (Farads, Ohms) before calculating time constants to get Hertz correctly.

analysis method (nodal vs. Miller approximation)?

- Did they ignore any capacitance? Why was it negligible?
- How did they handle the Miller effect?
- Can I reproduce the same steps on a different problem?

WHY STUDYING SOLUTIONS HELPS, BUT ONLY IF USED CORRECTLY

A solution manual for Chapter 11 can be a double-edged sword. Used passively—just copying answers—it teaches nothing. Used actively, it becomes a powerful learning tool. When you review a solution, ask yourself:

- Why did they choose that particular

In the **Fundamentals of Microelectronics Solution Chapter 11**, you will often see multiple ways to solve the same problem. Compare them. For example, some solutions compute the exact transfer function, while others use the method of time constants to get an approximate bandwidth. Understanding the trade-offs between accuracy and simplicity

is a valuable skill for real-world design.

INTEGRATING THEORY WITH PRACTICAL IC DESIGN

Frequency response is not just an academic exercise. In modern integrated circuits, operating frequencies range from megahertz to gigahertz. A designer must ensure that each stage in a chain has adequate bandwidth to avoid distorting the signal. The **Fundamentals of Microelectronics Solution Chapter 11** teaches you how to quickly estimate bandwidth using

simple hand calculations—a skill that is indispensable during the initial design phase.

Moreover, concepts from this chapter, such as pole splitting and compensation, are directly applied in operational amplifier design to ensure stability. When you later study feedback systems, you will revisit these ideas. Mastering Chapter 11 now lays the groundwork for more advanced topics like phase-locked loops, data converters, and RF front-ends.

ADDITIONAL RESOURCES
